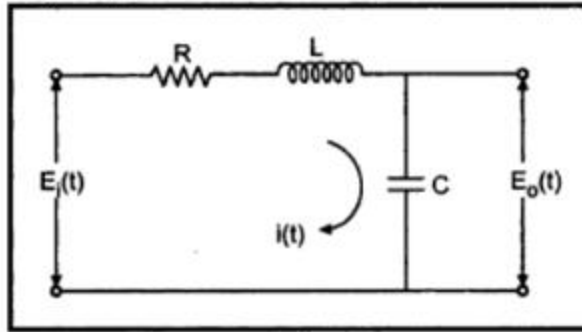


Ex.1. Find out the T.F. of the given network.



Sol. : Applying KVL we get the equations as,

$$E_i = iR + L \frac{di}{dt} + \frac{1}{C} \int idt \quad \dots (1)$$

$$i/p = E_i \quad ; \quad o/p = E_o$$

Laplace transform of $\int F(t) dt = \frac{F(s)}{s}$, neglecting initial conditions

and laplace transform of $\frac{df(t)}{dt} = sF(s)$... neglecting initial conditions

Take Laplace transform,

$$\therefore E_i(s) = I(s) \left[R + sL + \frac{1}{sC} \right]$$

$$\frac{I(s)}{E_i(s)} = \frac{1}{\left[R + sL + \frac{1}{sC} \right]} \quad \dots (2)$$

Now $E_o = \frac{1}{C} \int idt \quad \dots (3)$

$$\therefore E_o(s) = \frac{1}{sC} I(s)$$


$$\therefore I(s) = sC E_o(s) \quad \dots (4)$$

Substituting value of I(s) in equation (2)

$$\therefore \frac{sC E_o(s)}{E_i(s)} = \frac{1}{\left[R + sL + \frac{1}{sC} \right]}$$


$$\therefore \frac{E_o(s)}{E_i(s)} = \frac{1}{sC \left[R + sL + \frac{1}{sC} \right]} = \frac{1}{RsC + s^2 LC + 1}$$

So we can represent the system as

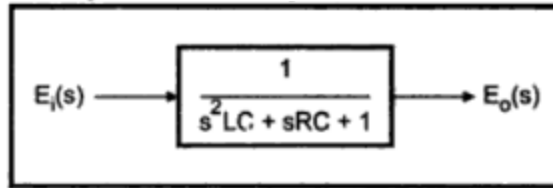

The characteristic equation is,
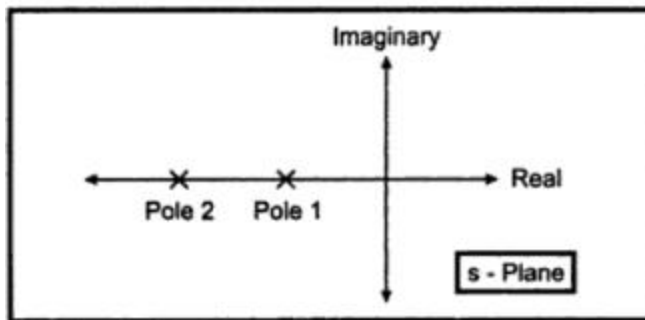
$$s^2 + s \frac{R}{L} + \frac{1}{LC} = 0$$




So system is 2nd order and the two poles are, $-\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{\sqrt{LC}}\right)^2}$

T.F. has no zeros.

Now if values of R, L and C selected are such that both poles are real, unequal and negative the corresponding pole-zero plot can be shown as in Fig.

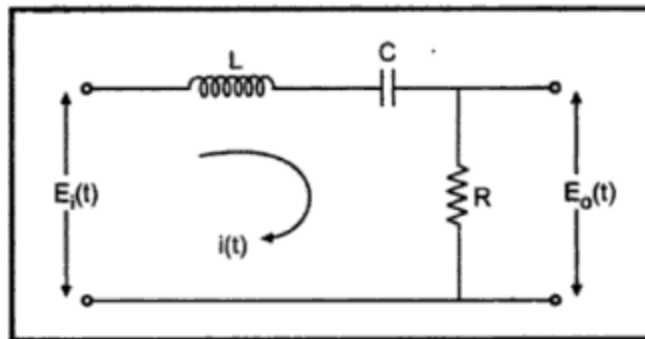Ex.2. Find out the T.F. of the given network



Sol. : Applying KVL we can write,

$$E_i(t) = L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt + i(t)R \quad \dots (1)$$

While $E_o(t) = i(t)R \quad \dots (2)$

Where $E_i(t) = \text{input}$ and $E_o(t) = \text{output}$

Taking Laplace of equations (1) and (2), neglecting the initial conditions.

$$E_i(s) = sLI(s) + \frac{1}{C} \frac{I(s)}{s} + RI(s) \quad \dots (3)$$

$$E_o(s) = I(s)R \quad \dots (4)$$

$\therefore E_i(s) = I(s) \left[sL + \frac{1}{sC} + R \right]$ from (3)

Substituting $I(s) = \frac{E_o(s)}{R}$ from (4) in the above equation we get,

$$E_i(s) = \frac{E_o(s)}{R} \left[sL + \frac{1}{sC} + R \right]$$

$\therefore E_i(s) = \frac{E_o(s)}{R} \times \left[\frac{s^2LC + 1 + sCR}{sC} \right]$

$\therefore \frac{E_o(s)}{E_i(s)} = \frac{sRC}{s^2LC + sRC + 1}$

Ex.3. The Laplace inverse of the transfer function in time domain of a certain system is e^{-5t} while its input is $r(t) = 2$. Determine its output $c(t)$.

Sol. ∴ Let $T(s)$ be the transfer function

$$L^{-1} [T(s)] = T(t) = e^{-5t} \quad \text{given}$$

$$r(t) = 2$$

But $c(t) \neq r(t) \times T(t)$,

it is mentioned earlier that $\frac{c(t)}{r(t)} = T(t)$ is not at all valid in time domain, so

$$c(t) \neq 2e^{-5t}$$

Hence the equation valid according to the definition of transfer function is,

$$T(s) = \frac{C(s)}{R(s)}$$

so $T(s) = L\{T(t)\} = L\{e^{-5t}\}$

$$= \frac{1}{s+5}$$

$$R(s) = \frac{2}{s}$$

$$\therefore \frac{1}{s+5} = \frac{C(s)}{\left(\frac{2}{s}\right)}$$

$$\therefore C(s) = \frac{2}{s(s+5)} = \frac{a_1}{s} + \frac{a_2}{s+5}$$

$$\therefore C(s) = \frac{0.4}{s} - \frac{0.4}{s+5}$$

Taking Laplace inverse of this equation

$$c(t) = 0.4 - 0.4 e^{-5t}$$

This is the required output expression.

Ex.4. The transfer function of a system is given by

$$T(s) = \frac{K(s+6)}{s(s+2)(s+5)(s^2+7s+12)}$$

Determine i) Poles ii) Zeros iii) Characteristic equation and iv) Pole-zero plot in s-plane.

Sol. :

i) **Poles** are the roots of the equation obtained by equating denominator to zero i.e. roots of

$$s(s+2)(s+5)(s^2+7s+12) = 0$$

$$\text{i.e. } s(s+2)(s+5)(s+3)(s+4) = 0$$

So there are 5 poles located at

$$s = 0, -2, -5, -3 \text{ and } -4$$

ii) **Zeros** are the roots of the equation obtained by equating numerator to zero i.e. roots of

$$K(s+6) = 0$$

$$\text{i.e. } s = -6$$

There is only one zero.

iii) Characteristic equation is one, whose roots are the poles of the transfer function. So it is


$$s(s+2)(s+5)(s^2+7s+12) = 0$$

$$\text{i.e. } s(s^2+7s+10)(s^2+7s+12) = 0$$


$$\text{i.e. } s^5 + 14s^4 + 71s^3 + 154s^2 + 120s = 0$$

iv) **Pole-zero plot**

This is shown in the Fig.

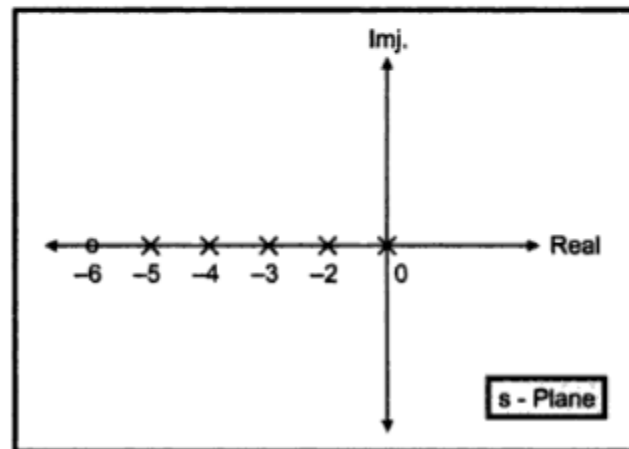


Ex.5. Find $V_o(s) / V_i(s)$

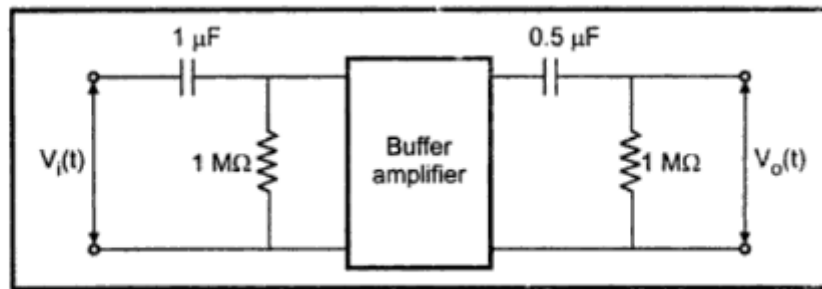


Assume gain of buffer amplifier as 1.

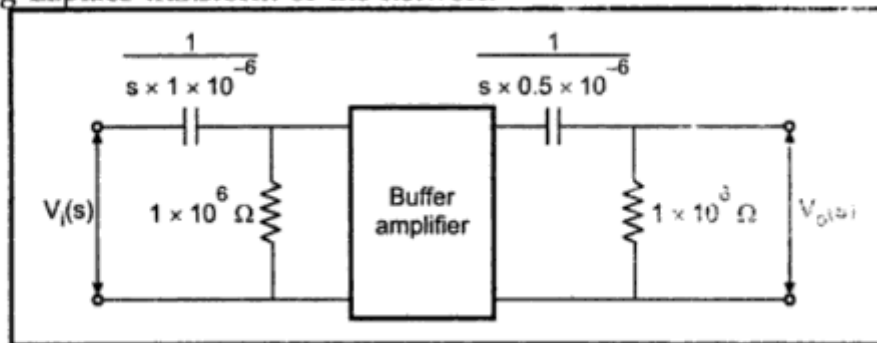Sol. : Taking Laplace transform of the network



Let us divide the network into two parts

Part 1)

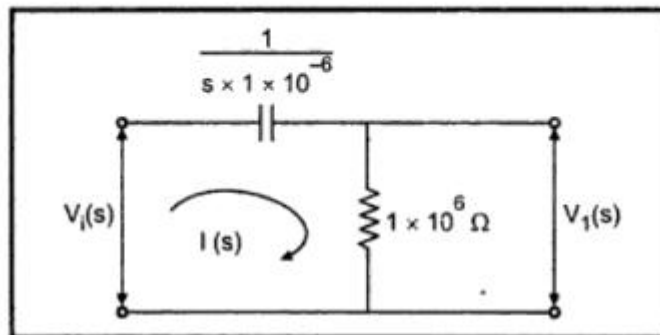

Applying KVL

$$V_i(s) = \frac{1}{s \times 10^{-6}} I(s) + 1 \times 10^6 I(s) \quad \dots (1)$$


$$V_1(s) = 1 \times 10^6 I(s) \quad \dots (2)$$

$$\therefore I(s) = \frac{V_1(s)}{1 \times 10^6}$$

Substituting in (1) $V_i(s) = \left[\frac{10^6}{s} + 10^6 \right] I(s) = \left[\frac{10^6 + s 10^6}{s} \right] \left[\frac{V_1(s)}{10^6} \right]$

$\therefore \frac{V_1(s)}{V_i(s)} = \frac{s}{s+1}$

Part 2)

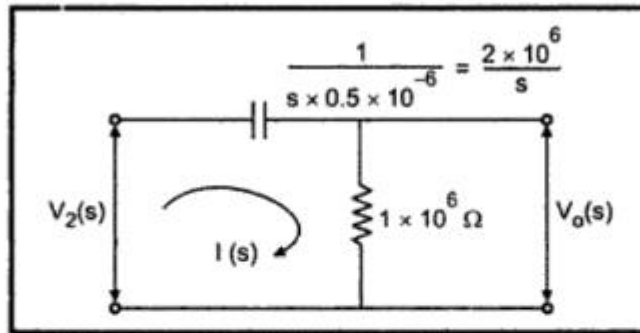

$\therefore V_2(s) = I(s) \left[\frac{2 \times 10^6}{s} + 1 \times 10^6 \right] \dots (1)$

$V_0(s) = I(s) 1 \times 10^6 \dots (2)$

$\therefore I(s) = \frac{V_0(s)}{10^6}$

Substituting in (1) $V_2(s) = \frac{V_0(s)}{10^6} \left[\frac{2+s}{s} \right] 10^6$

$\therefore \frac{V_0(s)}{V_2(s)} = \frac{s}{s+2}$

Now gain of buffer amplifier is 1 (unity)


$\therefore V_1(s) = V_2(s)$

$\therefore \left(\frac{s}{s+1} \right) V_i(s) = \frac{(s+2)}{s} V_0(s)$

$\therefore \frac{V_0(s)}{V_i(s)} = \frac{s^2}{(s+1)(s+2)}$

This is the required transfer function.

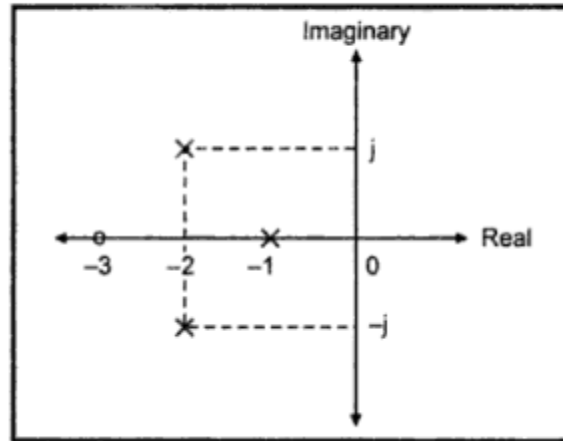Ex.6. Determine the transfer function if the d.c. gain is equal to 10 for the system whose pole-zero plot is shown below.



Sol. : From pole-zero plot given the transfer function has 3 poles at $s = 0$, $s = -1$, $-2+j$ and $-2-j$. And it has one zero at $s = -3$.

$$\begin{aligned} \therefore T(s) &= \frac{K(s+3)}{(s+1)(s+2+j)(s+2-j)} \\ &= \frac{K(s+3)}{(s+1)[(s+2)^2 - (j)^2]} \\ &= \frac{K(s+3)}{(s+1)[s^2 + 4s + 5]} \end{aligned}$$

Now d.c. gain is value of $T(s)$ at $s = 0$ which is given as 10.

$$\therefore \text{d.c. gain} = T(s)|_{s=0}$$


$$\therefore 10 = \frac{K \times 3}{1 \times 5}$$

$$\therefore K = \frac{50}{3} = 16.667$$




$$\therefore T(s) = \frac{16.667(s+3)}{(s+1)(s^2 + 4s + 5)}$$

This is the required transfer function.

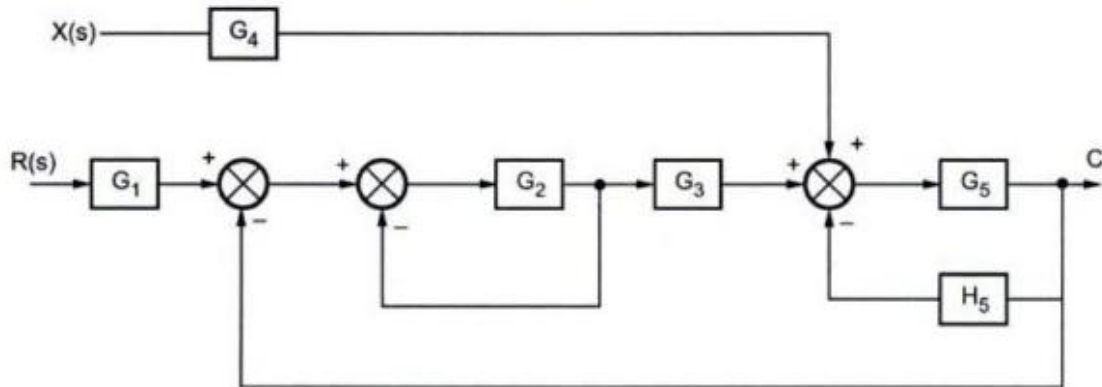Ex.7. Using block diagram reduction technique find the transfer function from each input to the output C for the system shown in the Fig.



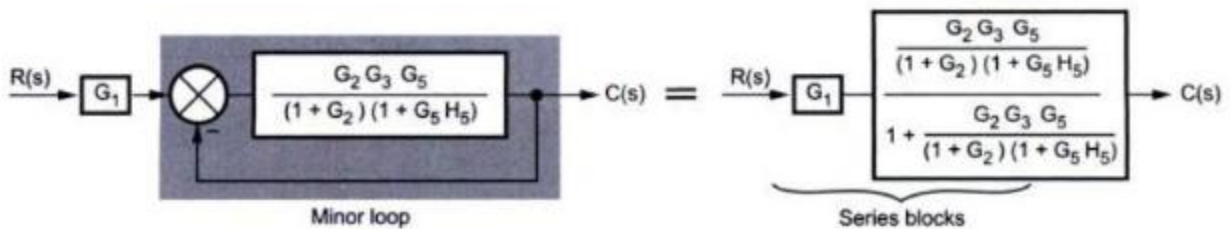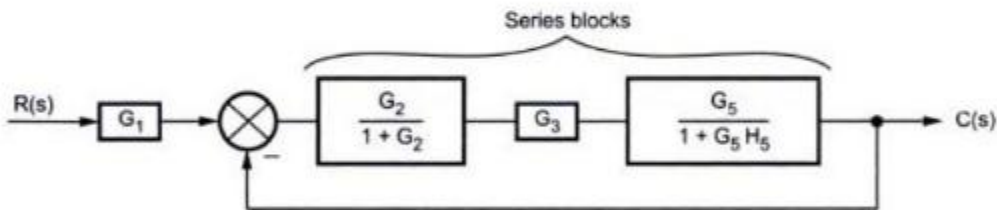
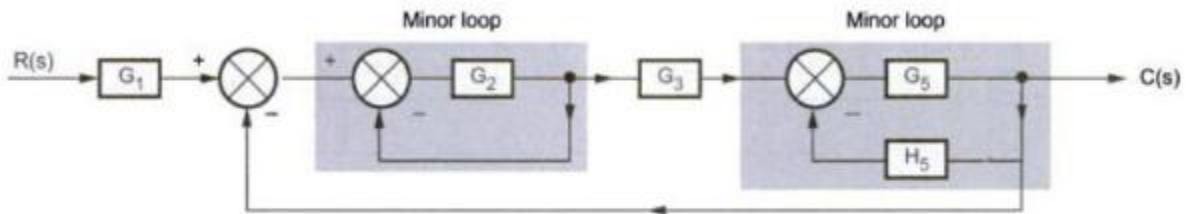
Solution : With $X(s) = 0$, block diagram reduces as,




\therefore

$$\frac{C(s)}{R(s)} = \frac{G_1 G_2 G_3 G_5}{1 + G_2 + G_5 H_5 + G_2 G_5 H_5 + G_2 G_3 G_5}$$

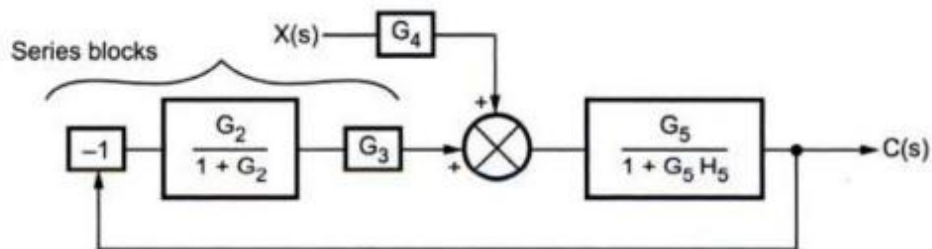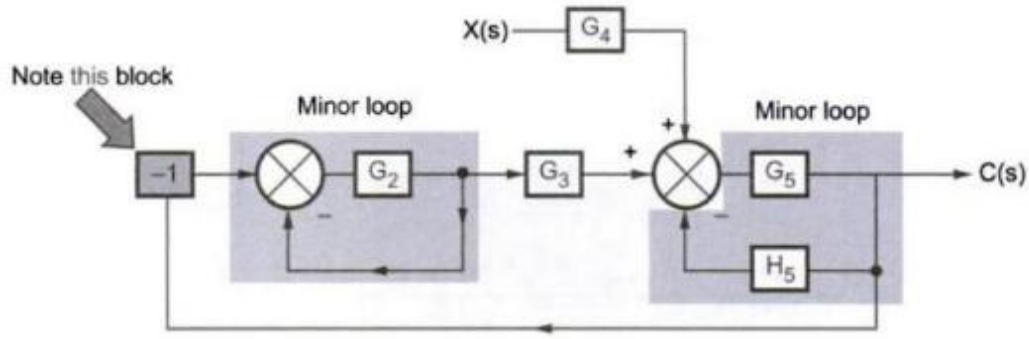With $R(s) = 0$, G_1 vanishes but minus sign at summing point must be considered by introducing block of -1 , as shown.




Rearranging the input - output we get,

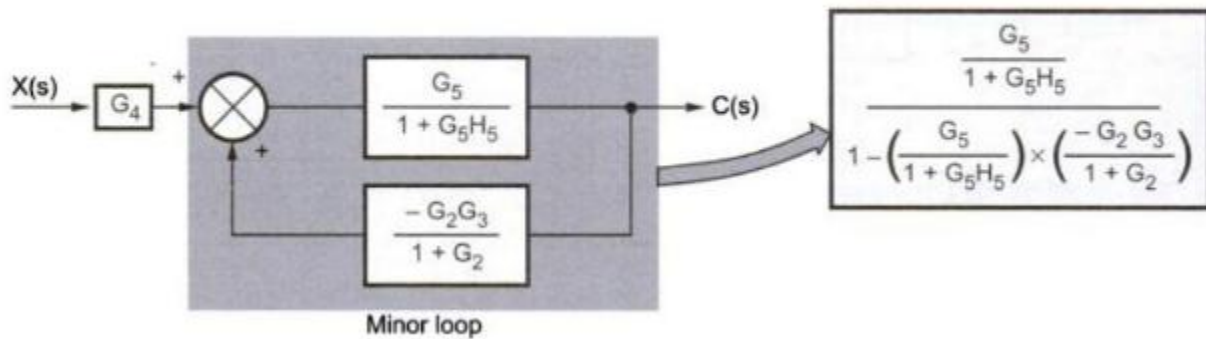


∴

$$\frac{C(s)}{X(s)} = \frac{G_4 G_5 (1 + G_2)}{1 + G_5 H_5 + G_2 + G_2 G_5 H_5 + G_2 G_3 G_5}$$

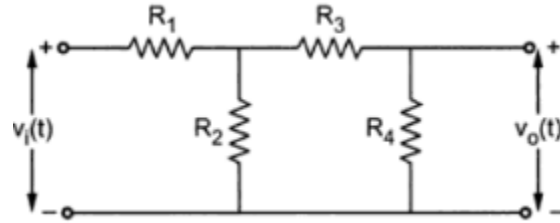Ex.8. Obtain the block diagram for the given electrical network.



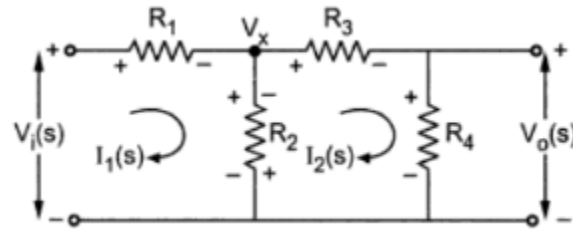Solution : Convert the given network into Laplace domain and assume the currents as shown in the Fig.




The KVL equations for the two loops are,

$$-I_1 R_1 - I_1 R_2 + I_2 R_2 + V_i = 0 \quad \text{i.e. } I_1 = V_i \left(\frac{1}{R_1 + R_2} \right) + I_2 \left(\frac{R_2}{R_1 + R_2} \right) \quad \dots (1)$$


$$-I_2 R_3 - I_2 R_4 - I_2 R_2 + I_1 R_2 = 0 \quad \text{i.e. } I_2 = I_1 \left[\frac{R_2}{R_2 + R_3 + R_4} \right] \quad \dots (2)$$

And $V_o = I_2 R_4 \quad \dots (3)$

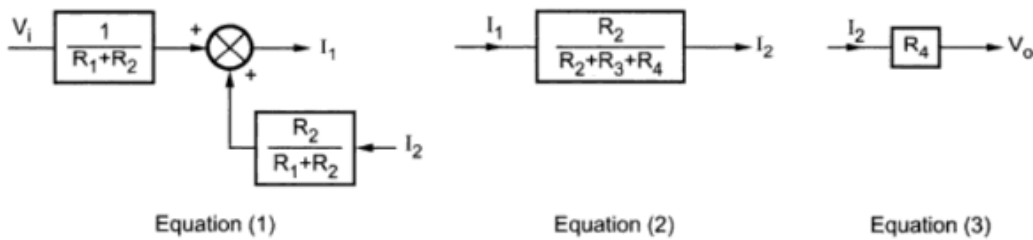The block diagrams for the three equations are,



Thus the overall block diagram is as shown in the Fig.

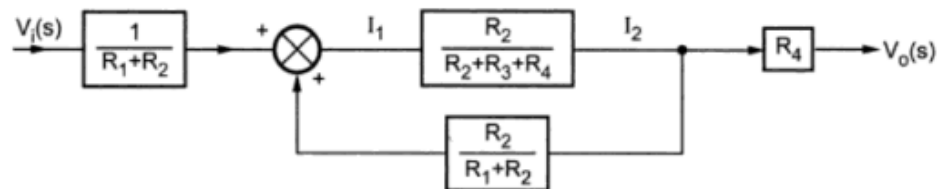

Ex.9. A unity feedback system has $G(s) = \frac{40(s+2)}{s(s+1)(s+4)}$.

Determine (i) Type of the system, (ii) All error coefficients and (iii) Error for ramp input with magnitude 4.

Solution : To determine type of system arrange $G(s)H(s)$ in time constant form.

$$\begin{aligned} G(s)H(s) &= \frac{40(s+2)}{s(s+1)(s+4)} = \frac{40(2)(1+0.5s)}{s(1+s)(4)(1+0.25s)} \\ &= \frac{20(1+0.5s)}{s(1+s)(1+0.25s)} \end{aligned}$$

Comparing this with standard form,

$$G(s)H(s) = \frac{K(1+T_1s)(1+T_2s)\dots\dots}{s^j(1+T_as)(1+T_bs)\dots\dots}$$

where $j =$ Type of system

$\therefore j = 1$ so given system is type 1 system.

Error coefficients :

$$1) K_p = \lim_{s \rightarrow 0} G(s)H(s) = \lim_{s \rightarrow 0} \frac{20(1+0.5s)}{s(1+s)(1+0.25s)} = \infty$$

$$2) K_v = \lim_{s \rightarrow 0} sG(s)H(s) = \lim_{s \rightarrow 0} \frac{20(1+0.5s)}{(1+s)(1+0.25s)} = 20$$

$$3) K_a = \lim_{s \rightarrow 0} s^2 G(s)H(s) = \lim_{s \rightarrow 0} \frac{s(1+0.5s) \cdot 20}{(1+s)(1+0.25s)} = 0$$

Now steady state error for ramp input is given by,

$$e_{ss} = \frac{A}{K_v}$$

where $A =$ Magnitude of ramp input

Here $A = 4$ and $K_v = 20$

$$\therefore e_{ss} = \frac{4}{20} = 0.2$$

Ex.10. : For unity feedback system,
 $G(s) = \frac{K}{s(1+0.4s)(1+0.25s)}$, find range of values of K, marginal value of K and frequency of sustained oscillations.

Solution : Characteristic equation, $1 + G(s)H(s) = 0$ and $H(s) = 1$

$$\therefore 1 + \frac{K}{s(1+0.4s)(1+0.25s)} = 0$$

$$s [1 + 0.65s + 0.1s^2] + K = 0$$

$$\therefore 0.1s^3 + 0.65s^2 + s + K = 0$$

s^3	0.1	1	From s^0 , $K > 0$
s^2	0.65	K	From s^1 ,
s^1	$\frac{0.65 - 0.1K}{0.65}$	0	$0.65 - 0.1K > 0$ $\therefore 0.65 > 0.1K$
s^0	K		$\therefore 6.5 > K$

\therefore Range of values of K, $0 < K < 6.5$.

The marginal value of 'K' is a value which makes any row other than s^0 as row of zeros.

$$\therefore 0.65 - 0.1 K_{\text{mar}} = 0$$

$$\therefore \boxed{K_{\text{mar}} = 6.5}$$

To find frequency, find out roots of auxiliary equation at marginal value of 'K'.

$$A(s) = 0.65s^2 + K = 0 ;$$

$$\therefore 0.65s^2 + 6.5 = 0 \quad \because K_{\text{mar}} = 6.5$$

$$s^2 = -10$$

$$s = \pm j 3.162$$

Comparing with $s = \pm j\omega$

$$\omega = \text{Frequency of oscillations}$$

$$= 3.162 \text{ rad/sec.}$$

Ex.11 : $s^6 + 2s^5 + 8s^4 + 12s^3 + 20s^2 + 16s + 16 = 0$. Check the stability of given characteristic equation using Routh's method.

Solution :

s^6	1	8	20	16	
s^5	2	12	16	0	
s^4	2	12	16	0	
s^3	0	0	0	0	← Special case 2
Row of zeros					

$$A(s) = 2s^4 + 12s^2 + 16 = 0$$

$$\frac{dA}{ds} = 8s^3 + 24s = 0$$

s^6	1	8	20	16
s^5	2	12	16	0
s^4	2	12	16	0
s^3	8	24	0	0
s^2	6	16	0	
s^1	2.67	0		
s^0	16			

No sign change, so system may be stable. But as there is row of zero, system will be (i) marginally stable or (ii) unstable. To examine this solve $A(s) = 0$.

$$2s^4 + 12s^2 + 16 = 0$$

$$s^4 + 6s^2 + 8 = 0$$

Put $s^2 = y$

$$\therefore y^2 + 6y + 8 = 0$$

$$y = -6 \pm \frac{\sqrt{36 - 32}}{2}$$

$$= -3 \pm 1 = -2, -4$$

$$\therefore s^2 = -2 \quad \text{and} \quad s^2 = -4$$

$$\therefore s = \pm j\sqrt{2} \quad \text{and} \quad s = \pm j2$$

Nonrepeated roots on imaginary axis. Hence system is marginally stable.

